

CSE460 - LAB 01

Name: F.M. Ashfaq

ID: 20101327

Section: 05


Problem statement: Write a Verilog code to implement the AOI-32 gate and verify it with the timing diagram in Quartus.

Code:

```
module aoi32(a, b, c, d, e, y1);
    input a, b, c, d, e;
    output y1;
    assign y1 = ~((a & b & c) | (d & e));
endmodule
```

Simulation report:

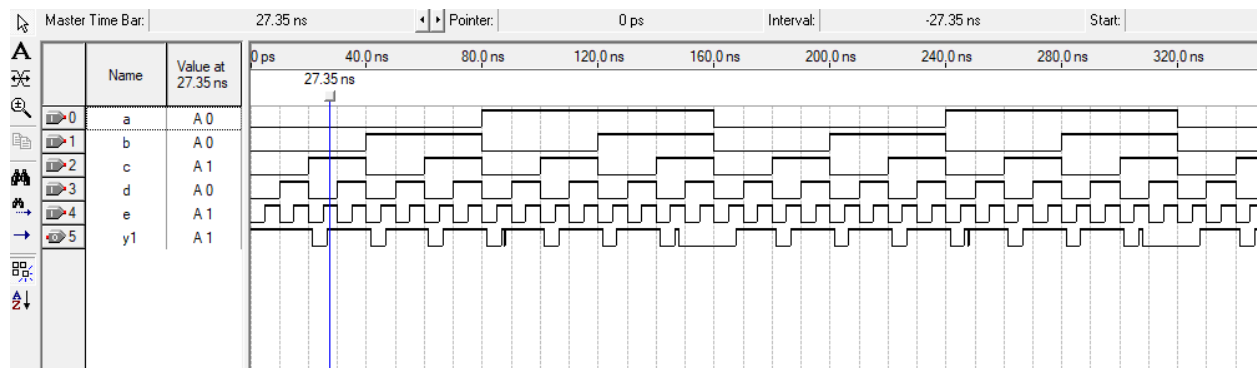
Waveform we will get when we set the clock of e to 10ns, d to 20ns, c to 40ns, b to 80ns and a to 160ns:



Truth table:

| a | b | c | d | e | $a.b.c$ | $d.e$ | $a.b.c + d.e$ | $\overline{a.b.c + d.e}$ |
|---|---|---|---|---|---------|-------|---------------|--------------------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |

RTL view:

 

Discussion: From the simulation report we can see that when we set all the input to 0, or when we get 0 from both of our AND gates, we will get output as 1. If we get 1 as an output from either of the AND gates then the output will be 0 as well as for any other combinations the output will be 0. Thus, the experiment is correct as it satisfies the truth table of AOI-32 gate.