

CSE 460: Quiz 2 Fall 2022 Solution. Set A

Question


i) Design a moore type sequence detector for 100

[State diagram only; overlapping allowed]

ii) Design a mealy type sequence detector for 01. clearly show state diagram, state table, state assigned table and by using k-map design the gate level circuit.

[overlapping allowed]

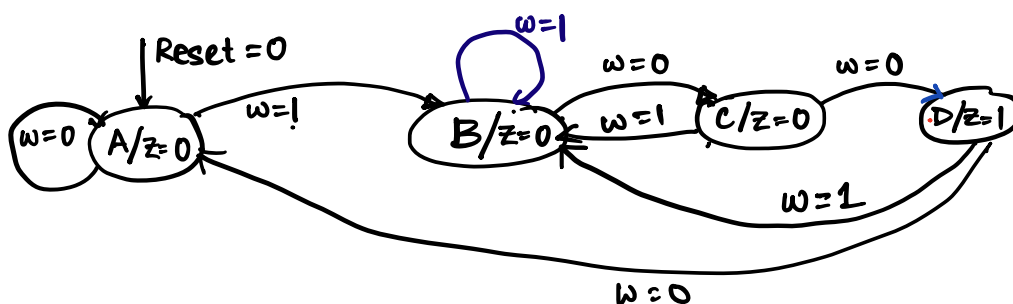
i) state diagram for 100 pattern detector. [Moore]



Test

w = 101001101000
z = 00001000001

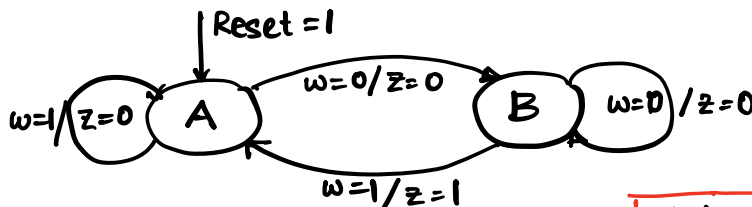ii) state diagram for 01 pattern detector. [Mealy]



Test

w = 101011001
z = 001010001

state Table

PS	Next state		Z	
	w=0	w=1	w=0	w=1
A	B	A	0	0
B	B	A	0	1

state assigned table

PS	Next state (y)		Z	
	w=0	w=1	w=0	w=1
0	1	0	0	0
1	1	0	0	1

K-MAPS

For Y,

w \ y	0	1
0	1	1
1	0	0

$$Y = \overline{w}$$


For Z,

w \ y	0	1
0	0	0
1	0	1


common values.

$$Z = wy$$

GATE Level circuit

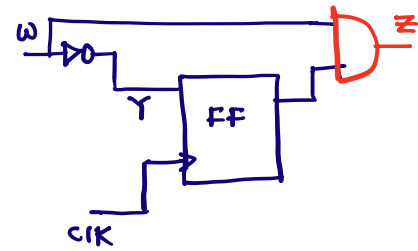

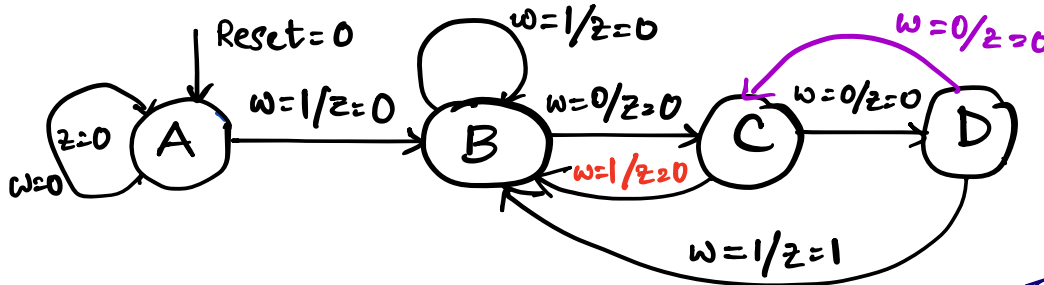i) If your pattern is 1001 [setA] {Mealy machine}



Test Sequence.

0	1	1	0	0	1	0	0	1	1	1	0	1	0	0	1
0	0	0	0	0	1	0	0	1	0	0	0	0	0	0	1

CSE 460: Quiz 2 Fall 2022 Solution.

Set B

Question


i) Design a moore type sequence detector for 011

[State diagram only; overlapping allowed]

ii) Design a mealy type sequence detector for 10. clearly show state diagram, state table, state assigned table and by using k-map, design the gate level circuit.

[overlapping allowed]

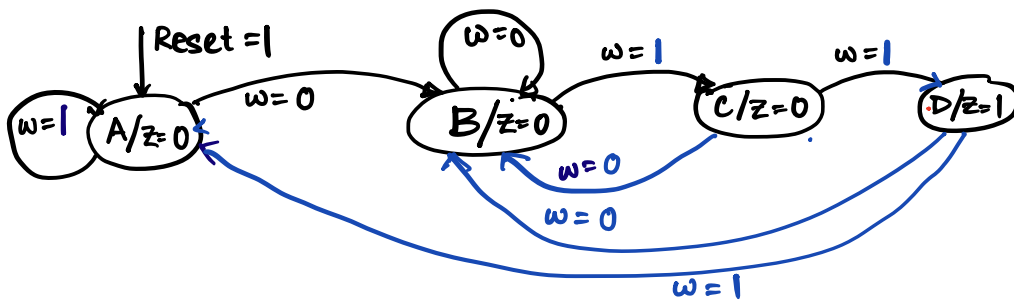
i) state diagram for 011 pattern detector. [Moore]



Test

w = 10011011010
z = 000010100

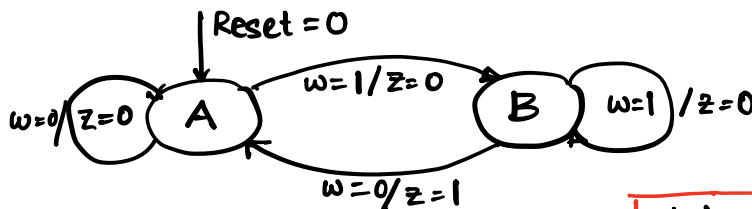ii) state diagram for 10 pattern detector. [Mealy]



Test

w = 101011001
z = 010100100

state Table

PS	Next state		Z	
	w=0	w=1	w=0	w=1
A	A	B	0	0
B	A	B	1	0

state assigned table

PS	Next state (y)		Z	
	w=0	w=1	w=0	w=1
0	0	1	0	0
1	0	1	1	0

K-MAPS

For Y ,

$w \backslash y$	0	1
0	0	0
1	1	1

$$Y = w$$

For Z ,

$w \backslash y$	0	1
0	0	1
1	0	0

↓ common value.

$$Z = \bar{w}y$$

GATE Level circuit

